

ONE WIRE KEY PAD



This page describes how to wire the output pins of a:

- seven pins, 3 columns * 4 rows key pad

and a

- four pins three button 3 x 1 keypad,

to a one wire analogue output.

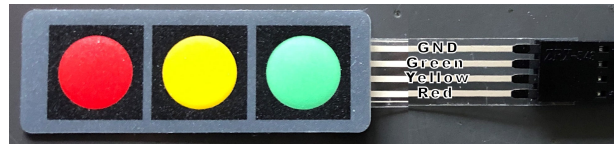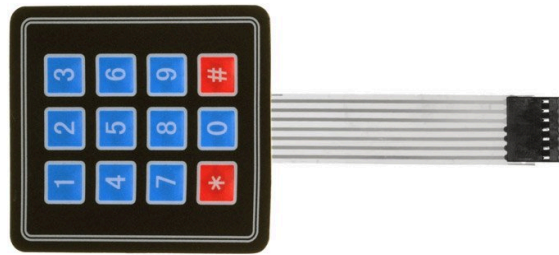

The addition with a few resistors converts the key pads to one wire and saves many digital pins at the cost one analogue pin. Libraries are not needed anymore and will save many memory bytes but lacking interrupt driven detection of operation of the key pad.

But processors are very fast and in many programs it is possible to check the buttons more than 1000 times a second. The three button key pad is a nice, flat, replacement of a rotary encoder saving three digital pins, a library and 1500 bytes.

3 X 4 key pad

Three different resistor resistances are used.

This page: <http://www.circuitbasics.com/how-to-set-up-a-keypad-on-an-arduino/> explains nicely how the key pad works.

There are many tutorials how to make a one-key wire keypad but or they use many resistors, make use of libraries or are hard to follow.

In the picture on the right one can see that by pressing a button a connection is made between a row and a column.

By choosing the right resistor combination the output will be different for every button.

5V is connected to C1 and ground after a 1.1 kilo-ohm resistor.


When 3 is pressed the current flows from R1 tot C3 and flows to a 1.1 kilo-ohm resistor resulting in a reading of 989 bits.



Pressing * R4 and C1 and connected resulting in a flow through all the resistors and a reading of 125 bits.

To discriminate between the buttons the difference between the difference button must be as large as possible.

Because resistors of identical resistance value will not have exact the same resistance measured, readings between modules will vary a little. In the Arduino source code the range per button is large enough to overcome these differences.

Key	470-470-4.7
*	125
0	142
#	166
7	265
4	297
1	338
8	359
5	420
2	506
9	531
6	707
3	989

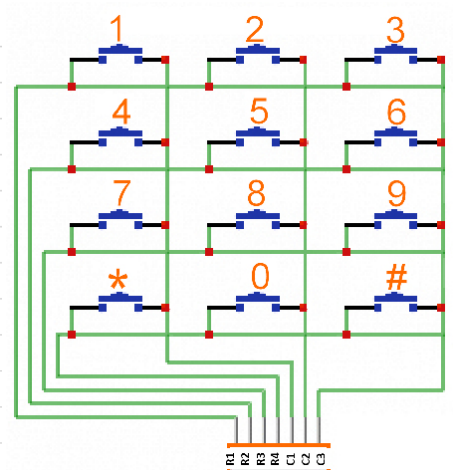

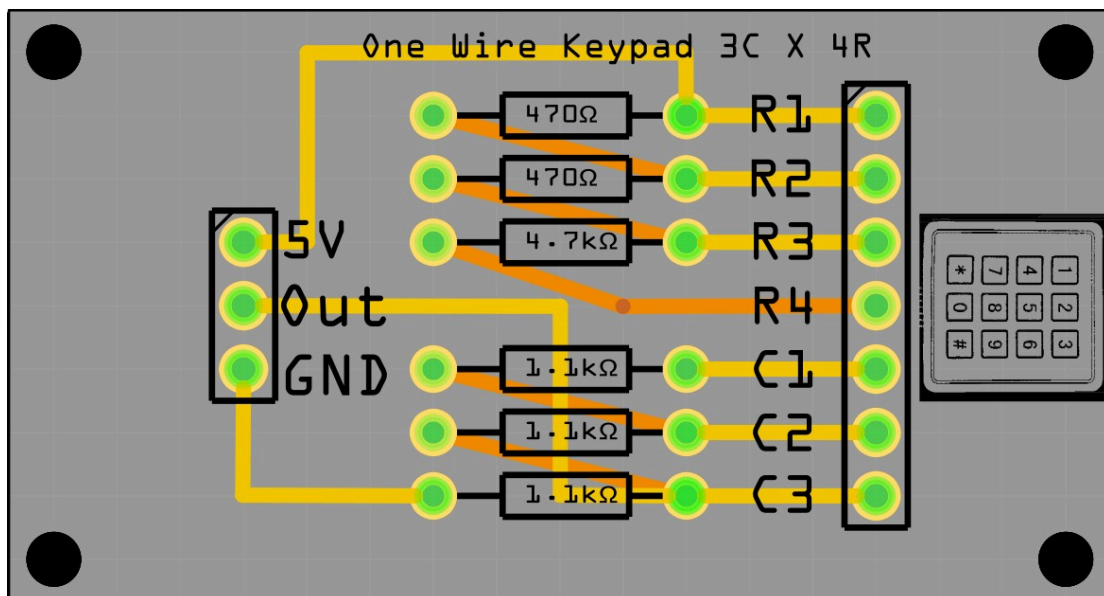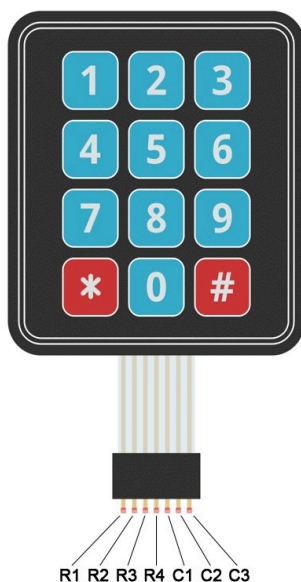

[OneWireKeypad.fzz](#) Fritzing file

Source code

[OneWireKeypad.ino](#)

Below the source code to read the key values

```

• int sensorPin = A0; // select the input pin for the potentiometer
  int ledPin = 13;    // select the pin for the LED
  int sensorValue = 0; // variable to store the value coming from the sensor
  byte keyvalue;

void setup()
{
  pinMode(ledPin, OUTPUT); // declare the ledPin as an OUTPUT:
  Serial.begin(9600);
  Serial.println("Started. Press a key");
}

void loop()
{
  sensorValue = analogRead(sensorPin); // read the value from the sensor:
  digitalWrite(ledPin, HIGH);          // turn the ledPin on
  switch(sensorValue)
  {
    case 0 ... 100: keyvalue = 13; break; // noise
    case 101 ... 132: keyvalue = 12; break; // *
    case 133 ... 154: keyvalue = 0; break; // 0
    case 155 ... 216: keyvalue = 11; break; // #
    case 217 ... 281: keyvalue = 7; break; // 7
    case 282 ... 318: keyvalue = 4; break; // 4
    case 319 ... 349: keyvalue = 1; break; // 1
    case 350 ... 390: keyvalue = 8; break; // 8
    case 391 ... 463: keyvalue = 5; break; // 5
    case 464 ... 519: keyvalue = 2; break; // 2
    case 520 ... 619: keyvalue = 9; break; // 9
    case 620 ... 848: keyvalue = 6; break; // 6
    case 849 ... 1023: keyvalue = 3; break; // 3
  }
  if(keyvalue<13) { Serial.println(keyvalue); delay(300); }
  digitalWrite(ledPin, LOW); // turn the ledPin off:
}


```

3 X 1 key pad

I use this key pad instead of a rotary encoder.



Key	1.1, 4.7, 4.7, 4.7 kOhm
Gnd	320
Green	450
Yellow	820
Red	1000

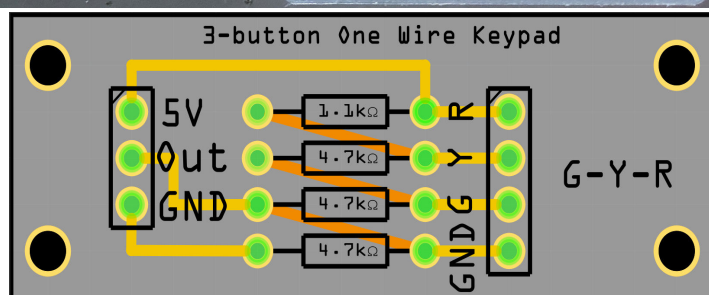

Source code: [OneWireKeyPad3x1.ino](#)

```
//-----  
// KEYPAD check for Onewire Keypad input with 5V and 1.1, 4.7, 4.7, 4.7 kOhm resistors  
//-----  
int sensorPin = A0;    // select the input pin for the potentiometer  
int ledPin = 13;       // select the pin for the LED  
int sensorValue = 0;   // variable to store the value coming from the sensor  
char keyvalue;  
char Key;  
  
void setup()  
{  
  pinMode(ledPin, OUTPUT); // declare the ledPin as an OUTPUT:  
  Serial.begin(9600);  
  Serial.println("Started. Press a key");  
}  
  
void loop()  
{  
  sensorValue = analogRead(sensorPin); // read the value from the sensor:  
  switch(sensorValue)  
  {  
    case 0 ... 385: keyvalue = 99;          break;          // noise  
    case 386 ... 635: keyvalue = -1; Key = 'G'; break;        // G  
    case 636 ... 910: keyvalue = 0; Key = 'Y'; break;         // Y  
    case 911 ... 1023: keyvalue = 1; Key = 'R'; break;         // R  
  }  
  if(keyvalue<2)  
  {  
    Serial.print(Key); Serial.print(" Read bits:"); Serial.println(sensorValue);  
    digitalWrite(ledPin, HIGH); // turn the ledPin on  
    delay(300);  
    digitalWrite(ledPin, LOW);  // turn the ledPin off:  
  }  
}
```

[FibonacciClock software V039 + libraries for one wire 4x3 keypad](#)

Ed Nieuwenhuys, July 2022, March 2021

November 2019

[< -- Back to start](#)